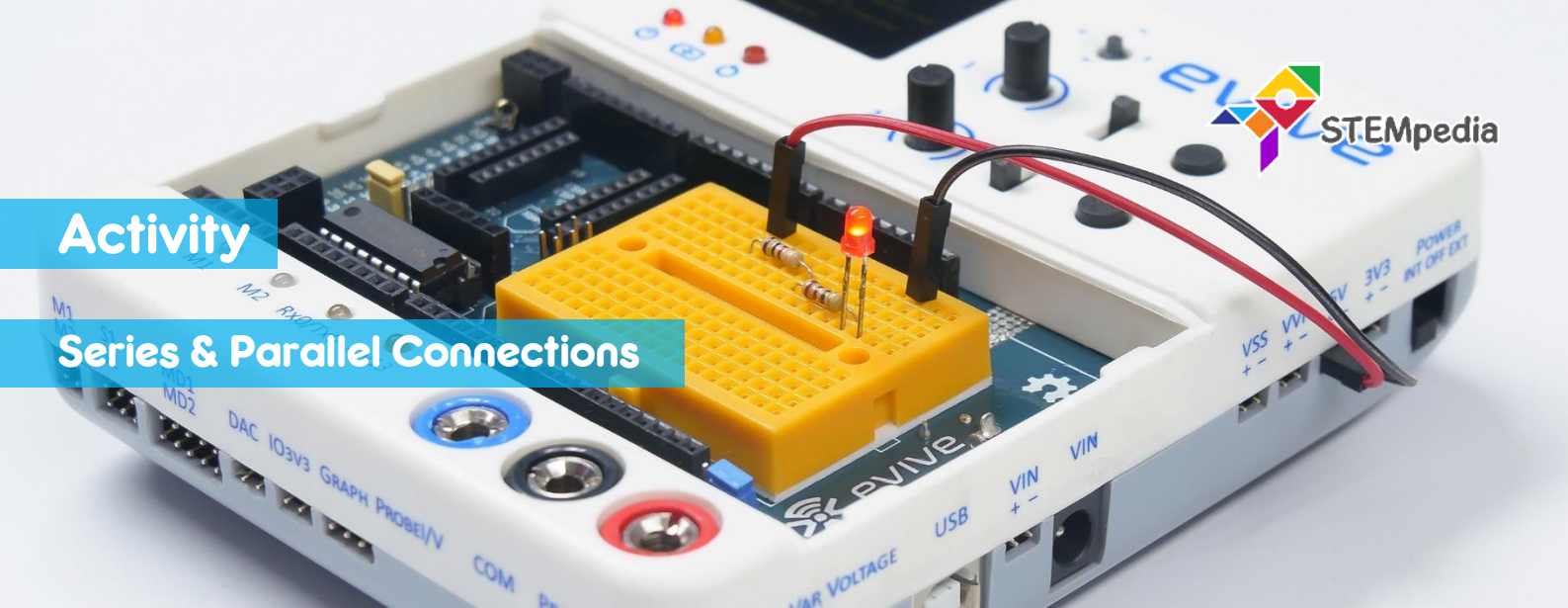


Activity

Series & Parallel Connections




In this activity, you will learn about series & parallel resistor circuits and its effect on the LED brightness.

COMPONENTS

LEDs, Resistor of different values, Jumper Cable and evive.

STEP-BY-STEP

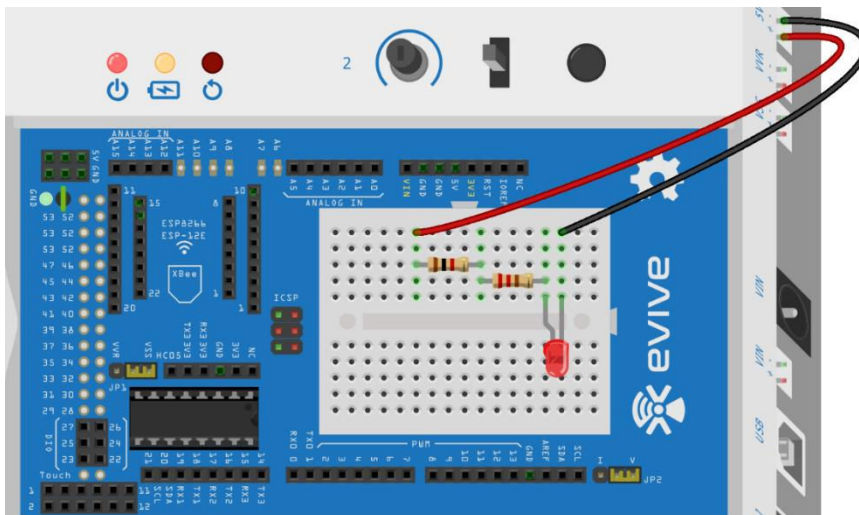1. **Series:** Make the following circuit on evive Breadboard for series resistors (Use two 220 Ohm resistors):



2. **Parallel:** Make the following circuit on evive Breadboard for parallel resistors (Use two 220 Ohm resistors):

